
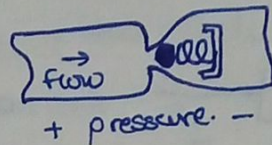




Lecture 13: Diode circuits - 1

Diode:

- It is a 2 terminal device

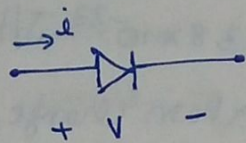

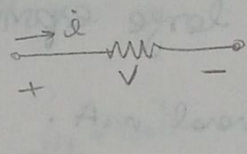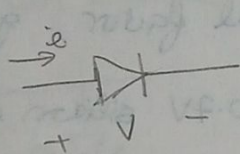
- A check valve presents a small resistance if pressure $p > 0$ but blocks the flow (presents large resistance) if $p < 0$.
- Similarly a diode presents a small resistance in the forward direction and a large resistance in the reverse direction.



$$R = R_{on} \text{ if } V > 0$$

$$R = R_{off} \text{ if } V < 0$$

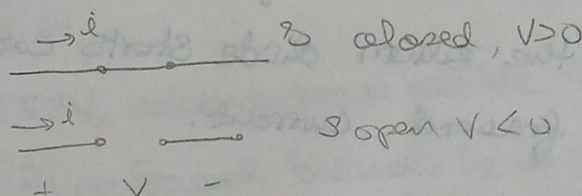- With $R_{on} = 0$ & $R_{off} = \infty$, the diode behaves like an ideal switch.




Forward bias: $i > 0 \text{ A}$, $V = 0 \text{ V} \rightarrow S$ is closed.



Reverse bias: $V < 0 \text{ V}$, $i = 0 \text{ A} \rightarrow S$ is open.

The diode is said to "block" the reverse applied voltage.

PARALLEL
CLIPPER
CIRCUIT

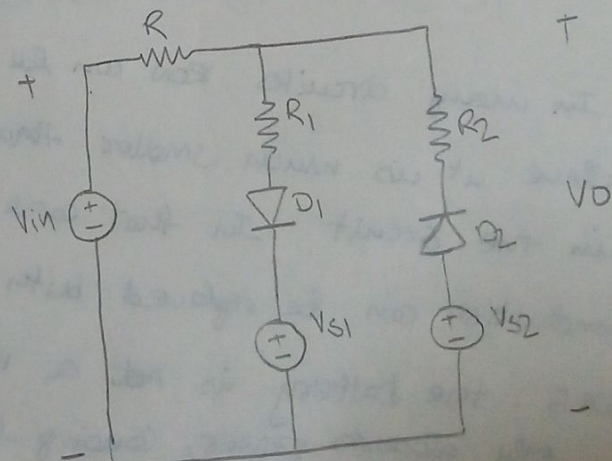

Schockley Diode Equation

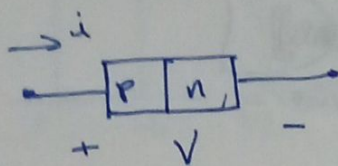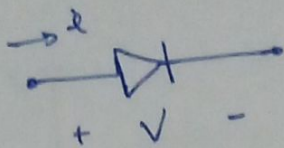

$$i = I_s [e^{V/V_T} - 1] \quad \text{where } V_T = k_B T / q$$

$$k_B = \text{Boltzmann's constant} \\ = 1.38 \times 10^{-23} \text{ J/K}$$


$$q = \text{electron charge} = 1.602 \times 10^{-19} \text{ coul}$$

$$T = \text{temperature in } ^\circ\text{K}$$

$$V_T = 25 \text{ mV at room Temp. } = 300 \text{ K.} \\ (\text{thermal voltage})$$

- I_s is called "reverse saturation current".
- It is normally very small, but since it gets multiplied by a large exponential factor, gives diode current in several mA. $V = 0.7 \text{ V}$ silicon diode
- The "turn on" voltage (V_{on}) of a diode depends on the value of I_s . V_{on} may be defined as the voltage at which the silicon diode starts carrying a substantial forward current.

Diode circuit model

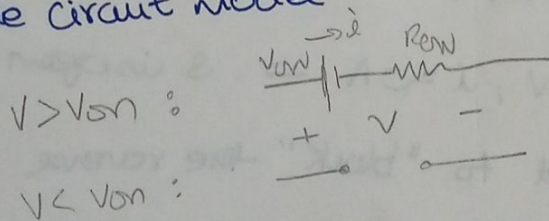


- In many circuits R_{on} can be neglected (assumed to be 0) since it is much smaller than the other resistances in the circuit. In that case, the diode in forward conduction can be replaced with simply a battery.

NOTE: the battery is not a "source" of power! It can only absorb power, causing heat dissipation.

Reverse Breakdown.


A real diode cannot withstand indefinitely large reverse voltages and "breaks down" at a certain voltage called "the breakdown voltage".

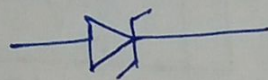- When the reverse bias $V_R > V_{BR}$, the diode allows a large amount of current. If the current is not constrained by the external circuit, the diode would get damaged.
- Diodes with high V_{BR} are generally used in power electronics applications and therefore also designed to carry a large forward current (tens or hundreds of Amps).




Zener diode.

Diode circuit example (Voltage limiter)

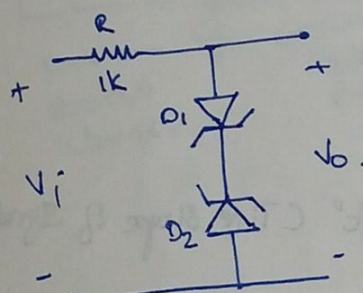

$$V_{on} = 0.7V \quad V_Z = 5V$$

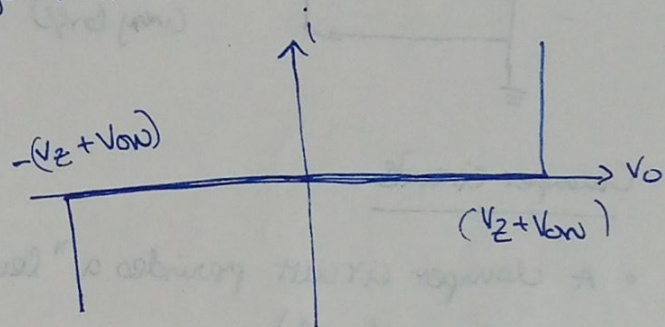


for $-5.7V < V_i < 5.7V$, no conduction is possible $\rightarrow V_o = V_i$




for $V_i > 5.7V$, D_1 is forward biased, D_2 is reverse-biased and $V_o = (V_{on} + V_Z)$. The excess voltage $(V_i - (V_{on} + V_Z))$ drops across R .

for $V_i < -5.7V$, D_2 is forward biased, D_1 is reverse biased

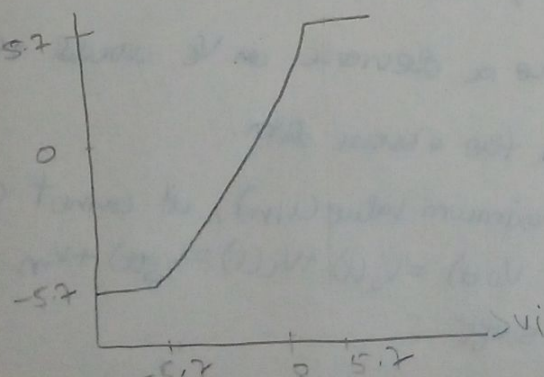
$V_o = -(V_{on} + V_Z)$. The excess voltage $(-V_i - (V_{on} + V_Z))$ drops across R .




Peak Detector (with $V_{on} > 0V$)

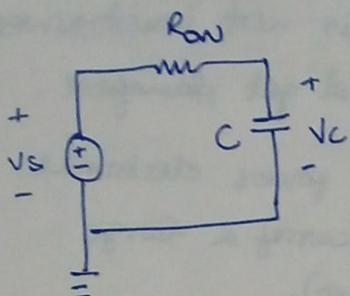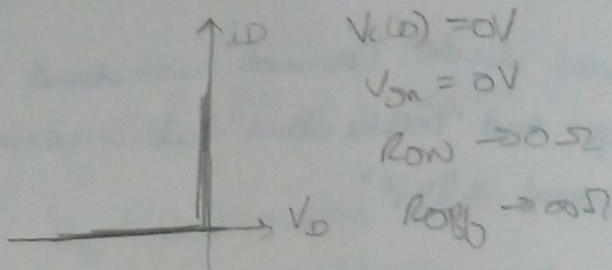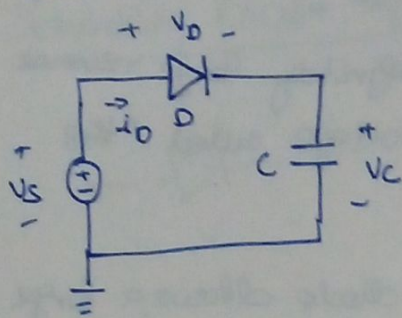

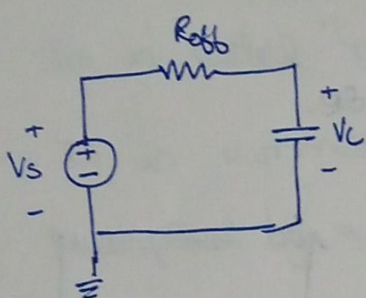$V_s > V_c$
 $\tau = R_{on}C$
 (very small)




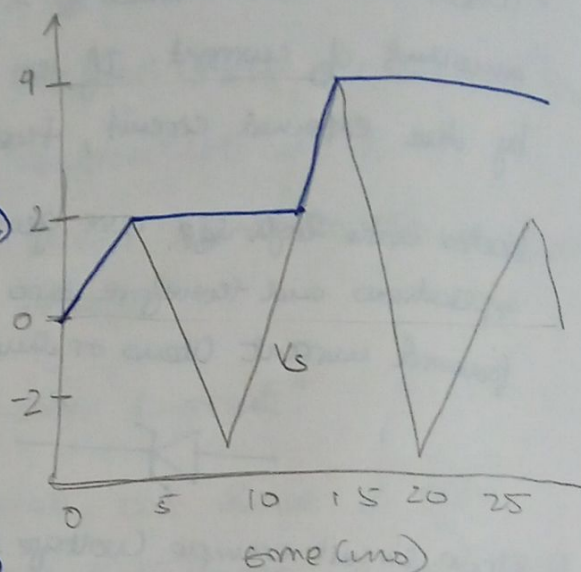
$V_s < V_c$
 $\tau = R_{off}C$
 (very large)



Clamper circuits

- A clamper circuit provides a "level shift" (The shape of signal is not altered).
- The shift could be positive or negative.

Positive Shift Clamper circuit.

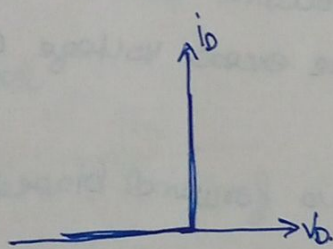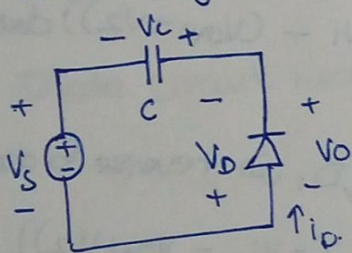


$V_s(t) = V_m \sin \omega t$
 $V_c(\omega) = 0V$
 $V_{on} = 0V$
 $R_{on} \rightarrow 0\Omega$ $R_{off} \rightarrow \infty\Omega$

When D conducts, the capacitor charges instantaneously since R_{on} is small. In this phase, $V_o > 0 \rightarrow V_c + V_s = 0 \rightarrow V_c = -V_s$.

V_c can only increase since a decrease in V_c would require the diode to conduct in the reverse dirn.

After V_c reaches its maximum value (V_m), it cannot change any more. We then have $V_o(t) = V_s(t) + V_c(t) = V_s(t) + V_m$
 i.e. positive level shift

Negative level shift clamping circuit.

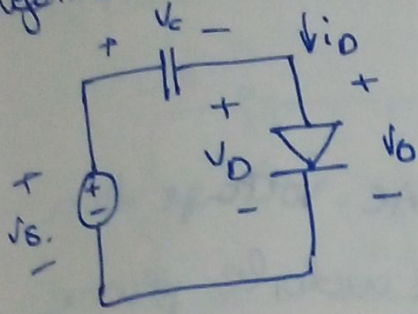

$$V_D = 0 \rightarrow V_C - V_S = 0 \rightarrow V_C = V_S$$

$$V_o(t) = V_S(t) - V_C(t) = V_S(t) - V_m(t)$$

\therefore negative level shift.

Voltage doubler (peak to peak detector).

