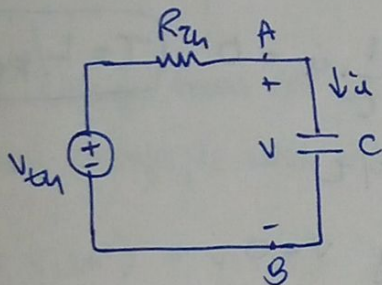


Week 2: Lecture 7

RC/RL circuits in time domain - 1

* RC circuits with DC sources

If all sources are DC (const.), $V_{TH} = \text{constant}$.



$$\text{KVL: } V_{TH} = R_{TH}i + V$$

$$V_{TH} = R_{TH}C \frac{dV}{dt} + V$$

$$\frac{dV}{dt} + \frac{V}{R_{TH}C} = \frac{V_{TH}}{R_{TH}C}$$

— Homogeneous soln.

$$\frac{dV}{dt} + \frac{1}{\tau}V = 0$$

$$\tau = R_{TH}C$$

↓
Time const.

$$V^{(h)} = K e^{-t/\tau}$$

— Particular soln → specific fn that satisfies differential equation.

Consider sinusoidal steady state;

time derivatives vanish at $t \rightarrow \infty \Rightarrow \frac{dV}{dt} = 0$

$$V^{(p)} = V_{TH}$$


$$V = V^{(h)} + V^{(p)} = K e^{-t/\tau} + V_{TH}$$

$$V(t) = A e^{-t/\tau} + B$$


where A & B are known constants of V.

$$i(t) = C \frac{dV}{dt} = C (A e^{-t/\tau}) \left(-\frac{1}{\tau}\right) = A' e^{-t/\tau}$$

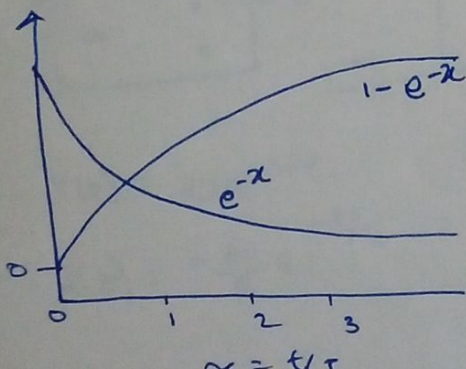@ $t \rightarrow \infty$, $i \rightarrow 0 \Rightarrow$ capacitor behaves like an open circuit.



* RL circuits with DC sources.

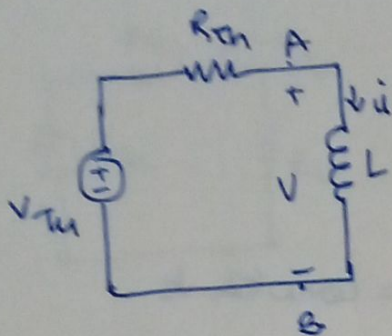

If all sources are DC (constant),
 $V_{TH} = \text{constant}$.

$$\text{KVL: } V_{TH} = R_{TH} i + L \frac{di}{dt}$$

Homogeneous solution

$$\frac{di}{dt} + \frac{1}{\tau} i = 0 \quad \boxed{\tau = L/R_{TH}}$$

$$i^{(h)} = k e^{-t/\tau}$$

particular soln $\Rightarrow t \rightarrow \infty$ making $v = 0$

$$i^{(p)} = V_{TH}/R_{TH}$$



$$i = i^{(h)} + i^{(p)} = k e^{-t/\tau} + V_{TH}/R_{TH}$$

$$i(t) = A e^{-t/\tau} + B \quad \text{where } A \text{ \& } B \text{ are known constants of } i.$$

$$v(t) = L \frac{di}{dt} = L \times A e^{-t/\tau} \left(-\frac{1}{\tau} \right) = A' e^{-t/\tau}$$

As $t \rightarrow \infty$, $v \rightarrow 0$ i.e. the inductor behaves like a short circuit.

* Can V_C change "suddenly"?

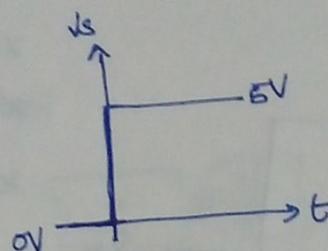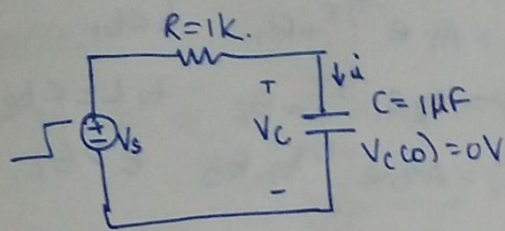

V_s changes from 0V (at $t=0^-$) to 5V (at $t=0^+$). As a result of this change, V_C will rise. How fast can V_C change?

$\Rightarrow V_C(0^+) = V_C(0^-) \Rightarrow$ A capacitor does not allow abrupt changes in V_C if there is a finite resistance in the circuit.

Say, V_C changes 1V in 1μs $\Rightarrow \frac{1V}{1\mu s} = 10^6 V/s$





$$i = C \frac{dV_C}{dt} = 1\mu F \times 10^6 \frac{V}{s} = 1A$$

$$R = 1000\Omega \rightarrow \text{Not possible!}$$

\Rightarrow Similarly an inductor does not allow abrupt changes in i_L .

* RC circuits: Charging and discharging transients





charging

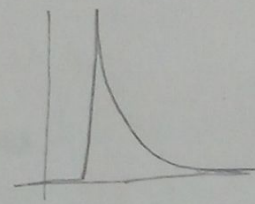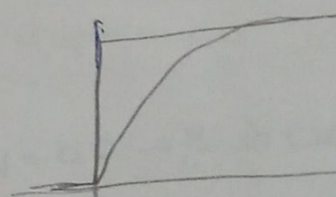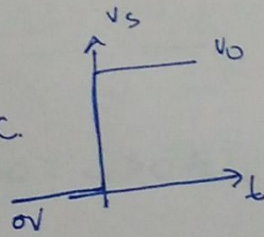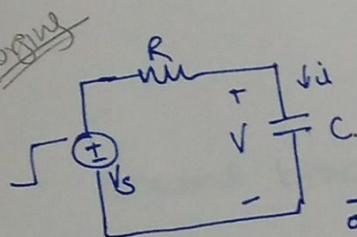

$$V(t) = V_0 [1 - e^{-t/\tau}]$$

$$i(t) = \frac{V_0}{R} e^{-t/\tau}$$

discharging

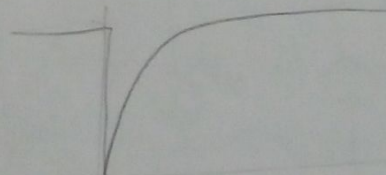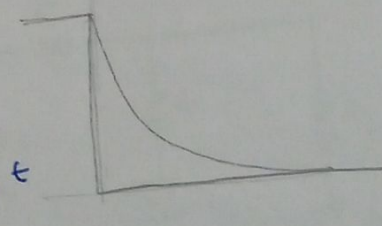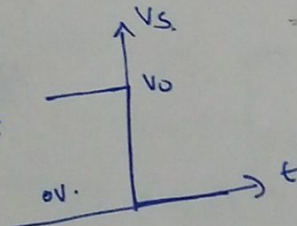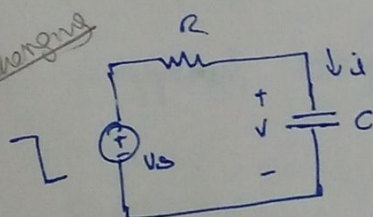


$$V(t) = V_0 e^{-t/\tau}$$

$$i(t) = -\frac{V_0}{R} e^{-t/\tau}$$

Lecture 9:

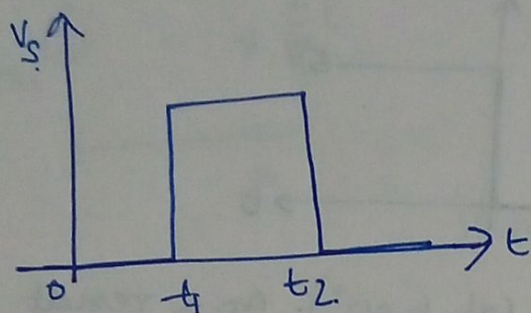Analysis of RC/RL circuits with a piece wise constant source



$$x(t) = A_1 e^{-t/\tau} + B_1 \quad t < t_1$$

$$x(t) = A_2 e^{-t/\tau} + B_2 \quad t_1 < t < t_2$$

$$x(t) = A_3 e^{-t/\tau} + B_3 \quad t > t_2$$

Steps: Identify $A_1 \dots A_3$, $B_1 \dots B_3$, τ , & $x(t)$ in each piece.

Calculate $v(t)$

Then use that to calculate $i(t)$

(or)

Calculate $i(t)$ from scratch.

How? — Consider to time instants $t(0^+)$ & $t(\infty)$

use that to find A & B.

Substitute back in Eqn with $v(t)$ or $i(t)$ value,

to get final Equation.